



College of Engineering,
Design and Computing
UNIVERSITY OF COLORADO **DENVER**


DEPARTMENT OF ELECTRICAL ENGINEERING
ELEC 3900: CIRCUIT DESIGN AND FABRICATION
SUMMER 2025


LAB#2
OP-AMP APPLICATIONS

KHALED ALOTAIBI



EXPERIMENT#1: Inverting Amplifier


1-

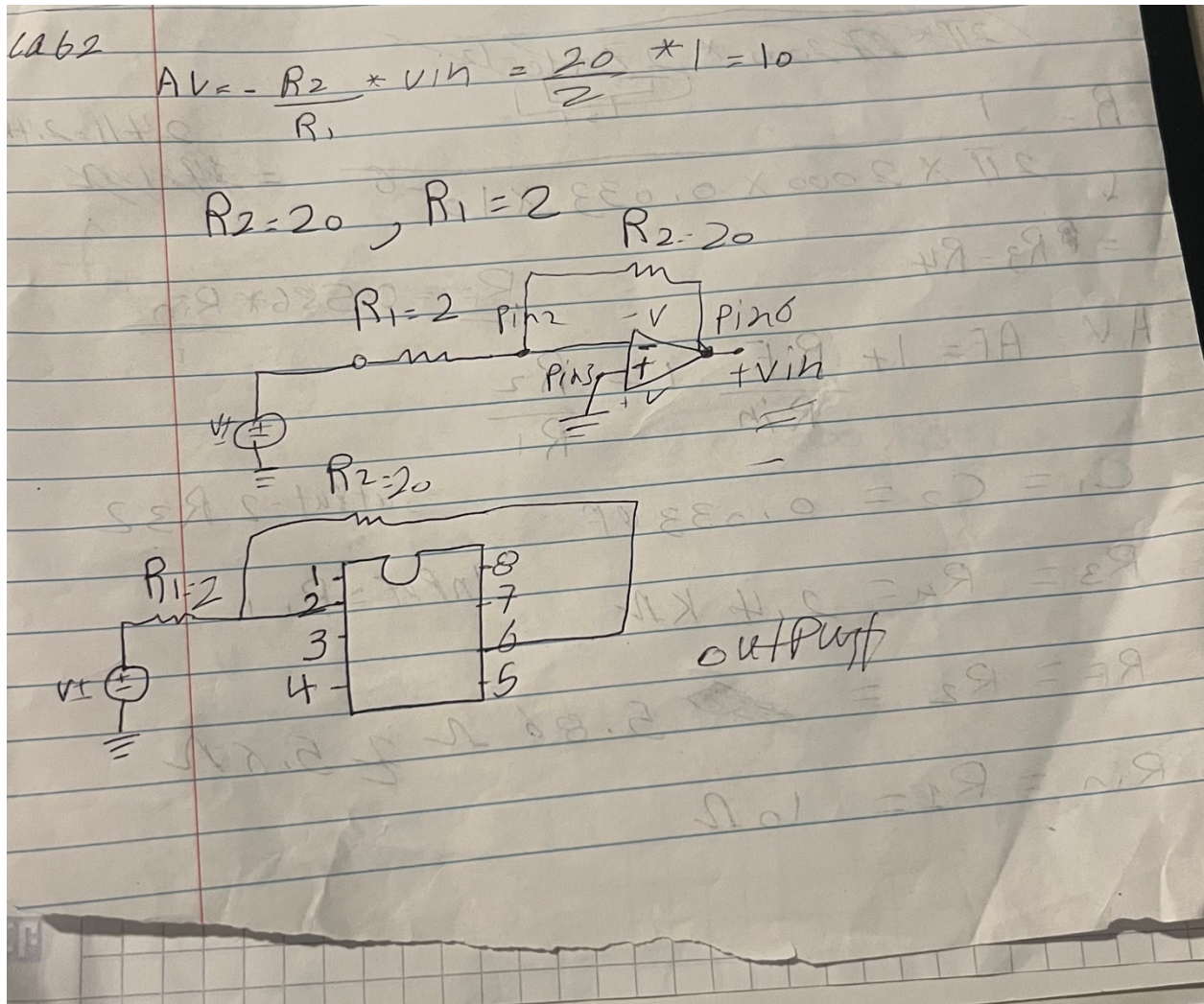


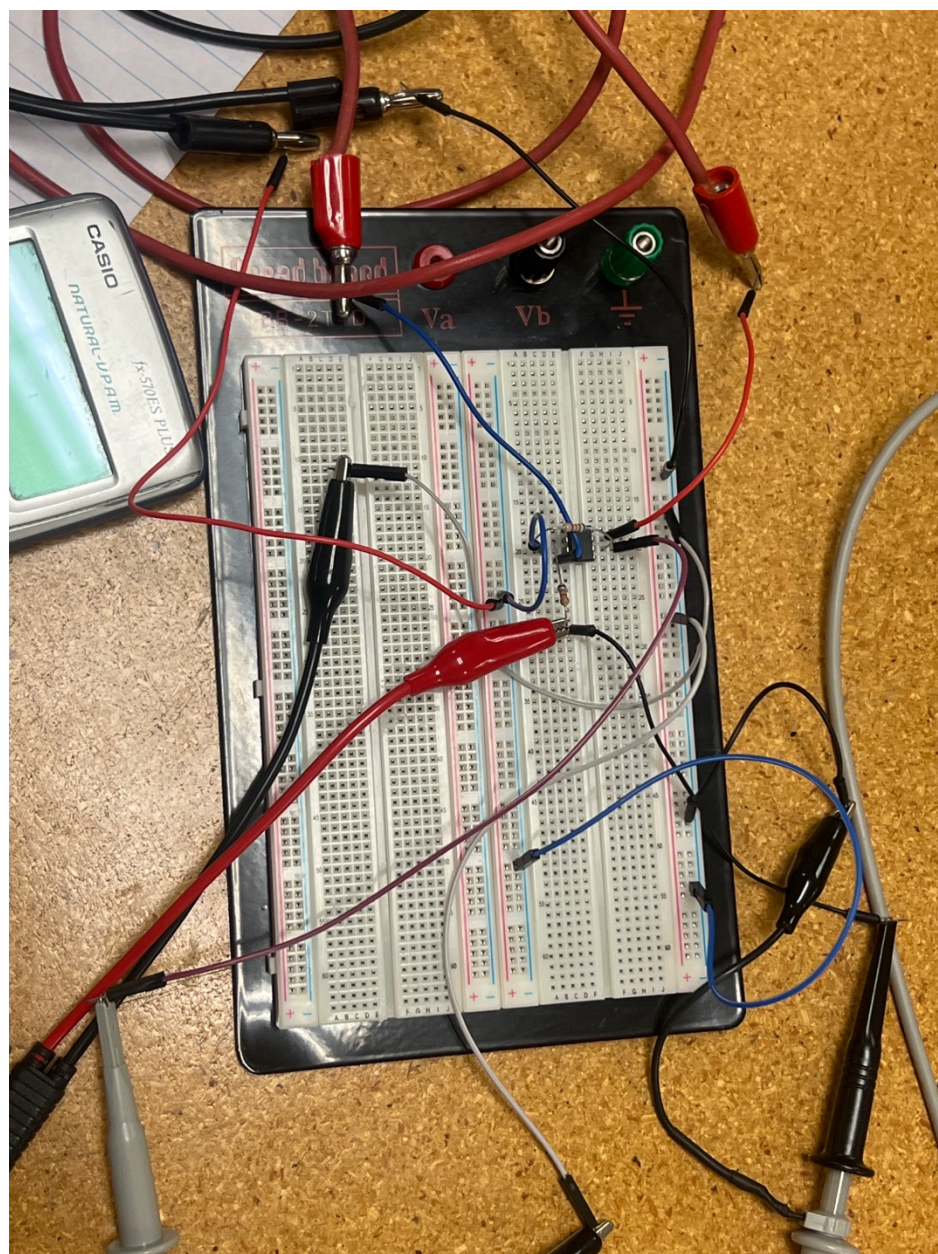


2-

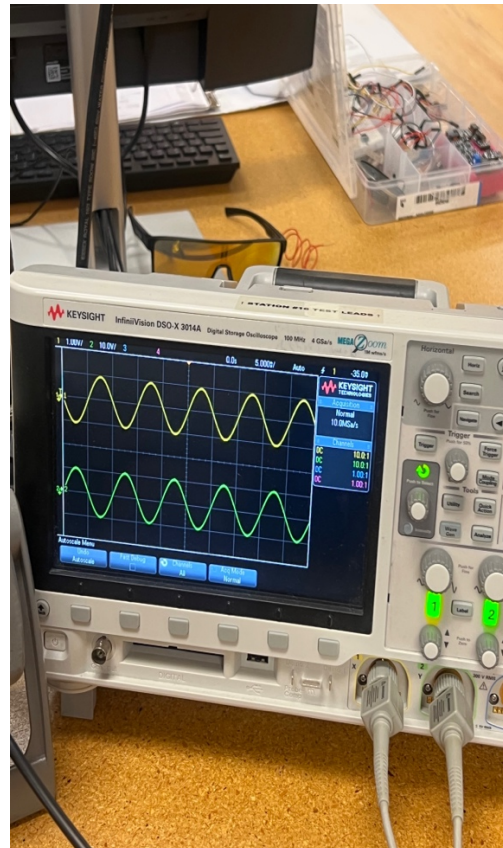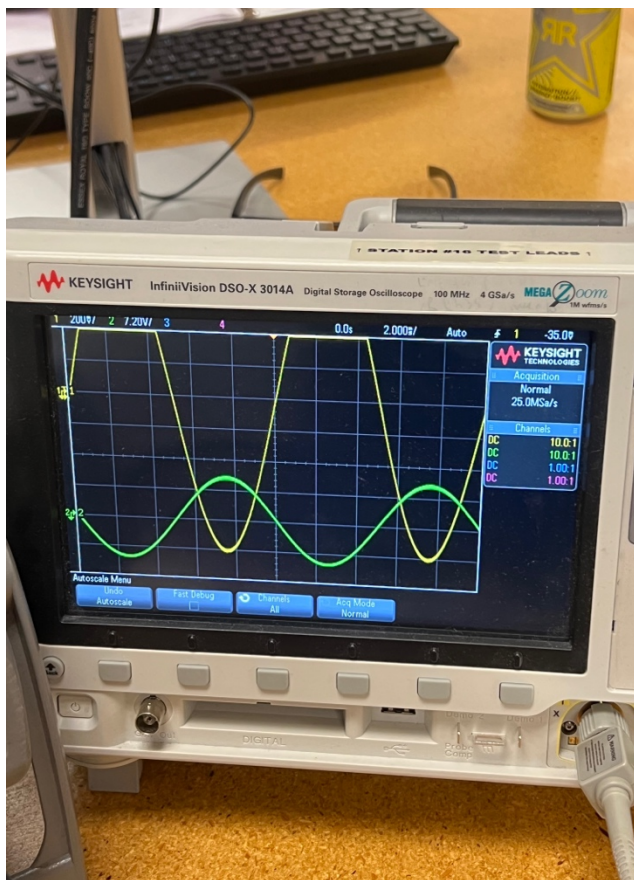

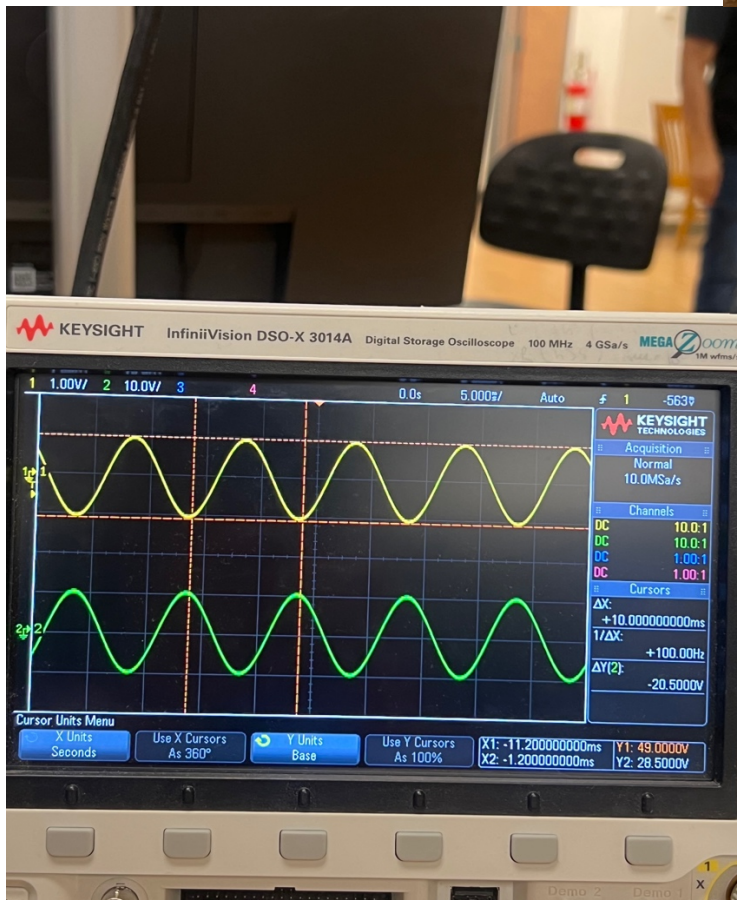

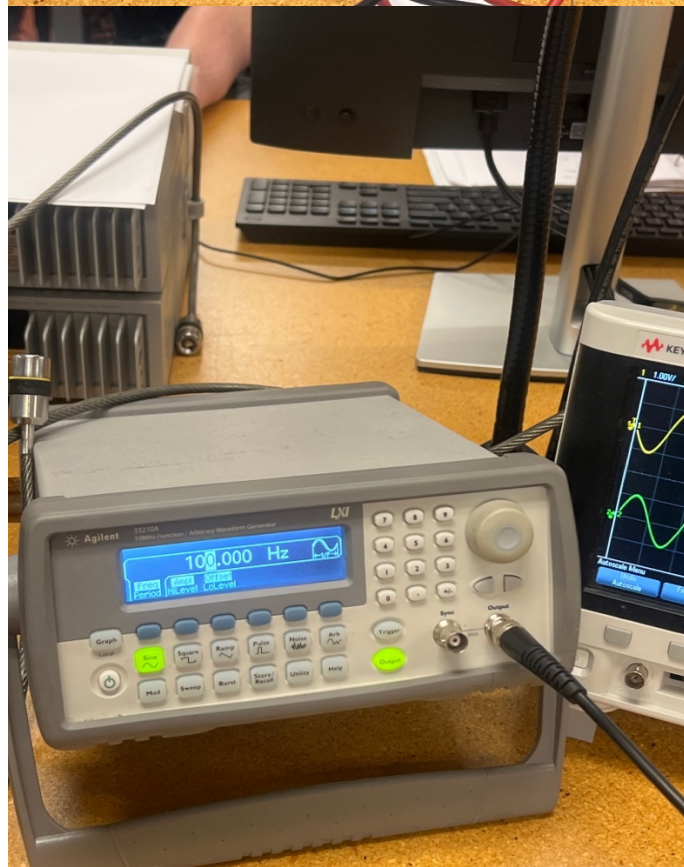

3-

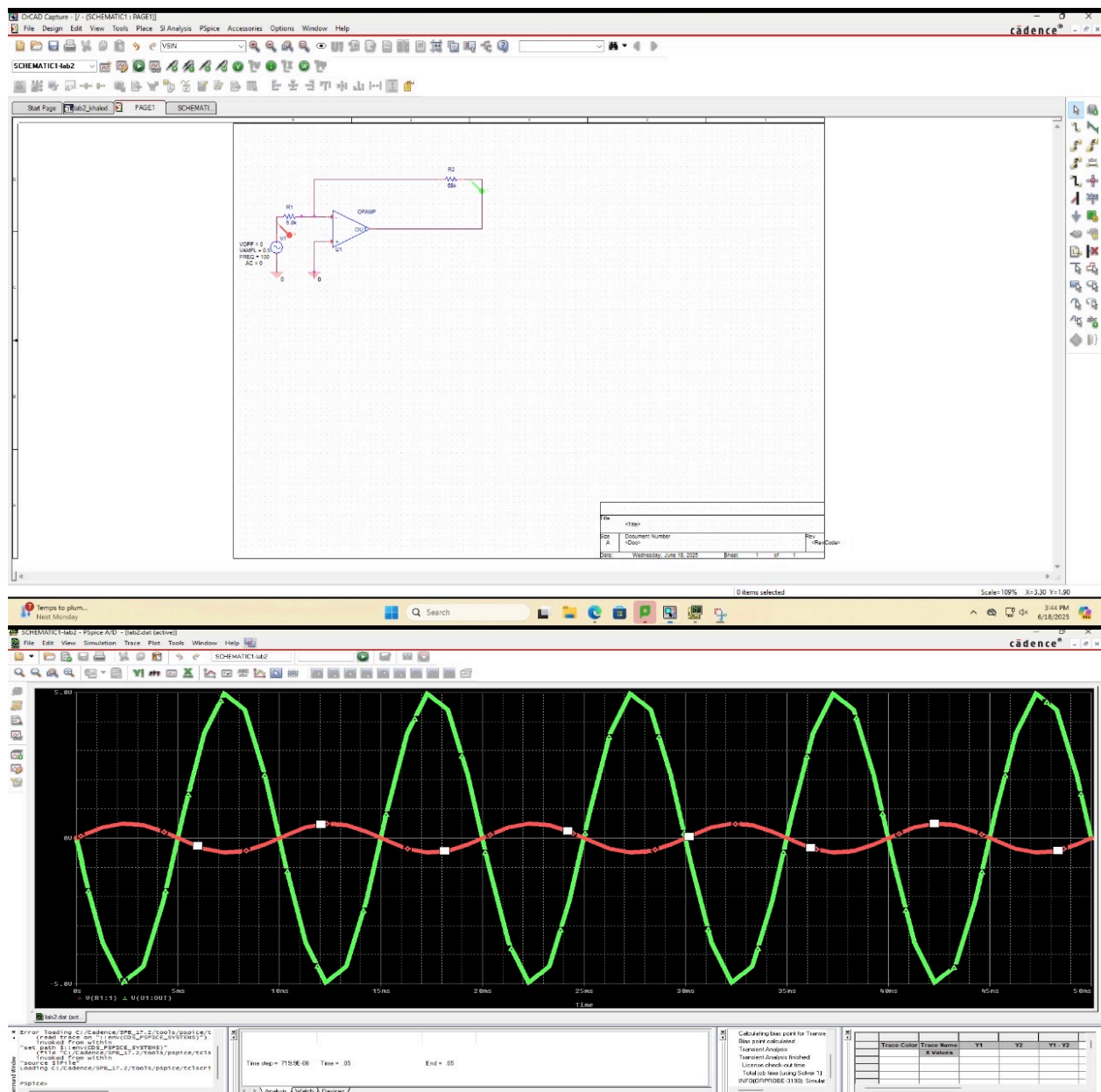


10/10

According to the manual calculation, the gain of inverting amplifier should be 10, and it can be seen in the oscilloscope and simulation that the output waveform is 10 times amplified. Then as the name suggests, output will be inverted as compared to input which means it will be 180 out of phase than the input which is also evident in the graphs.

EXPERIMENT#2: Non-inverting amplifier

1-

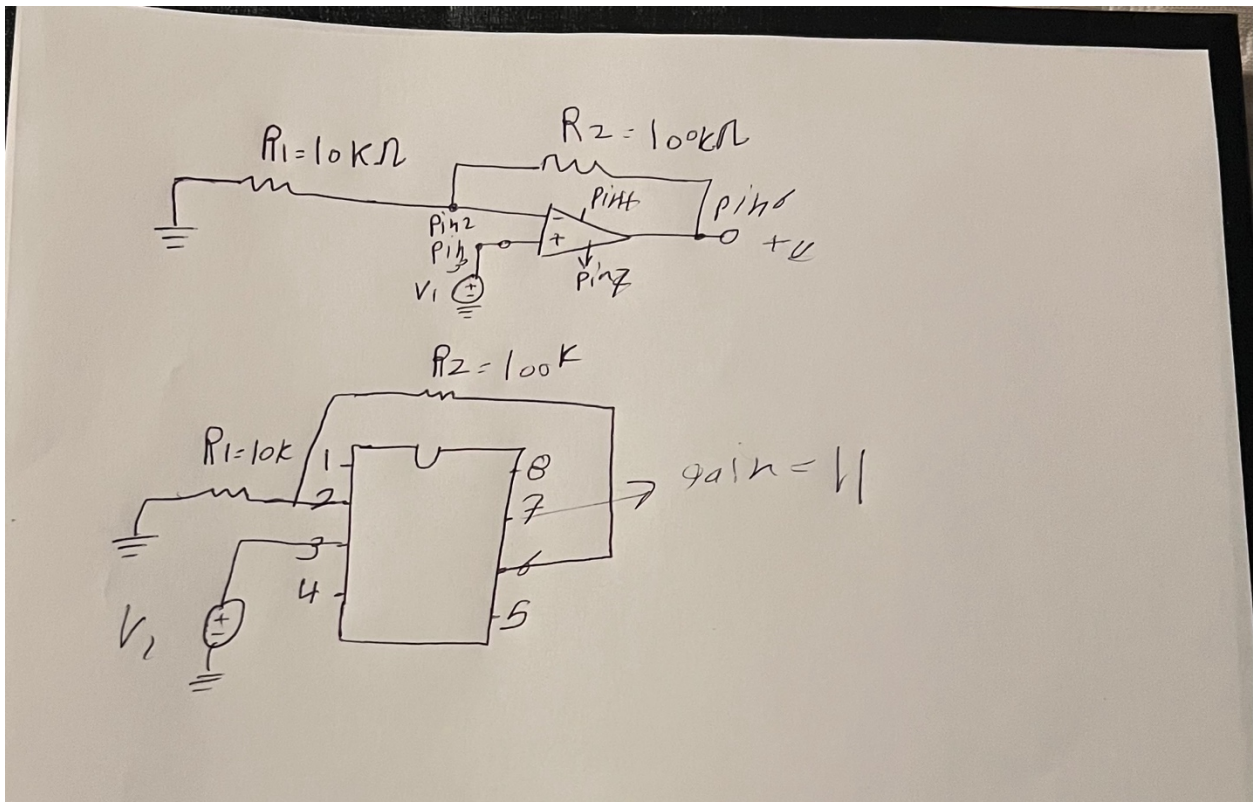

Lab 2 Experiment 2

$$A_V = \left\{ 1 + \frac{R_2}{R_1} \right\} V_{in}$$



non-inverting op-amp, gain of 11, $V_{in} = 1 \text{ V.P.P}$

$$f = 100 \text{ Hz}$$


$$R_2 = 100 \text{ k}\Omega, R_1 = 10 \text{ k}\Omega$$

$$11 = \left\{ 1 + \frac{100}{10} \right\} \times 1 = \left\{ 1 + 10 \right\} \times 1 = 11$$

2-

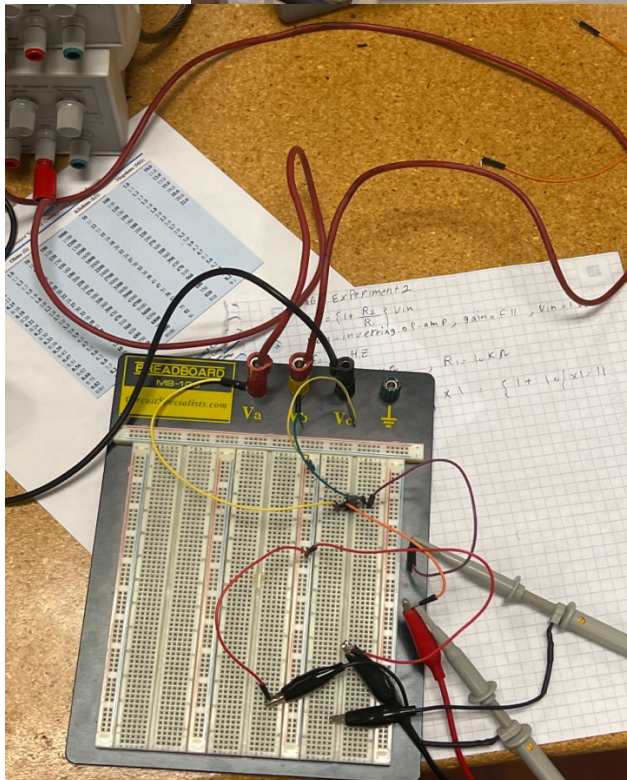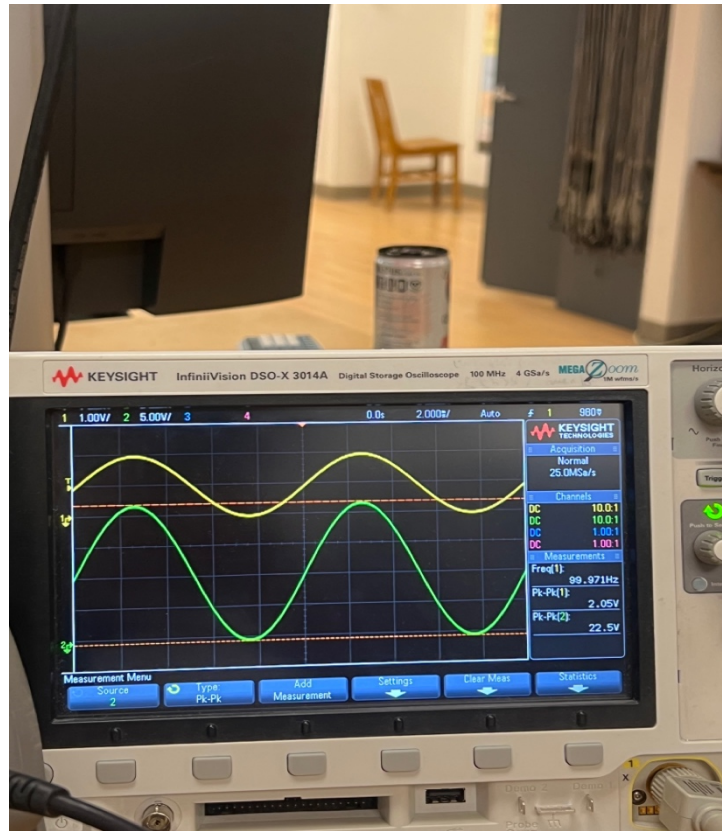

3-

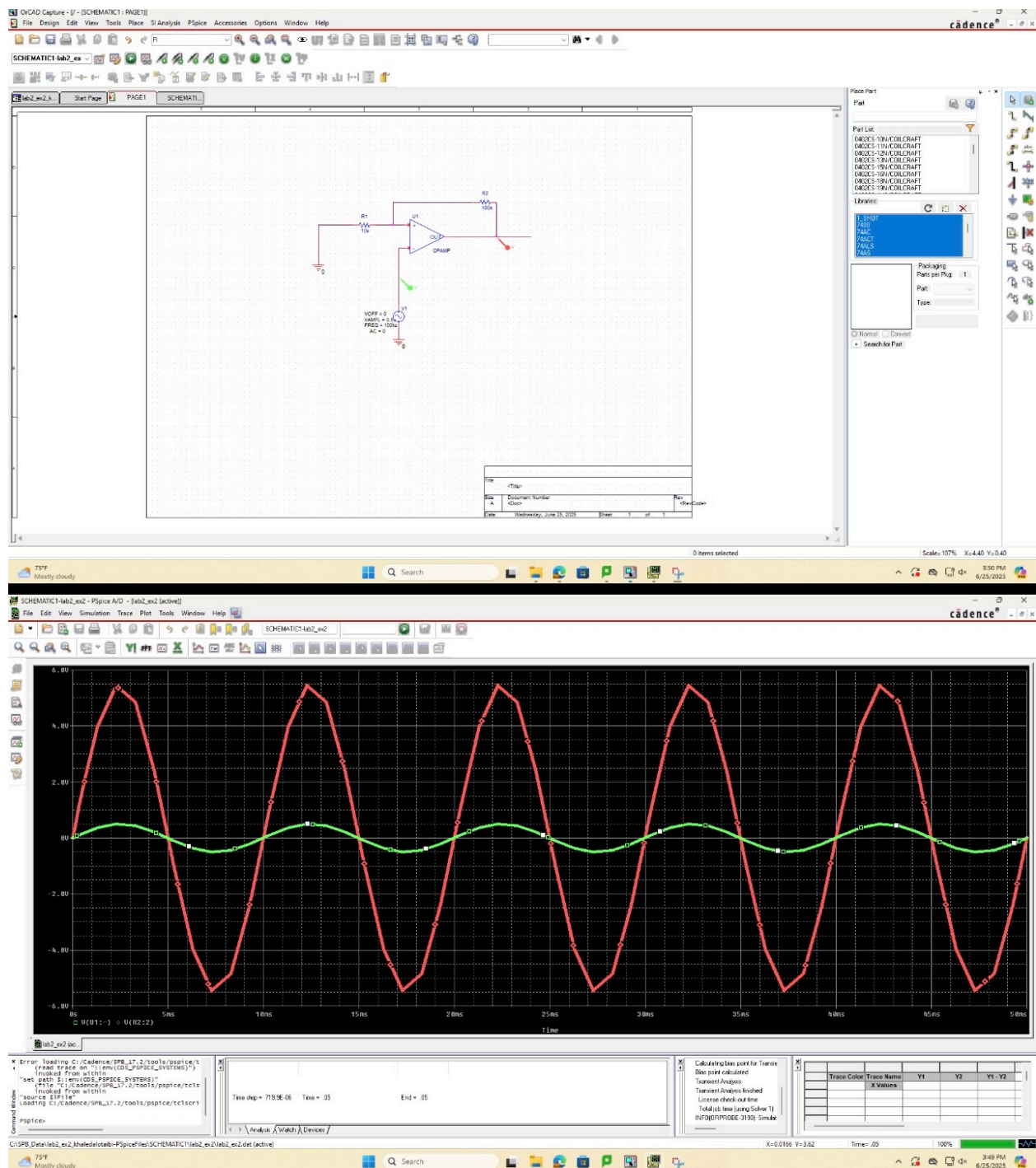

According to the manual calculation, the gain of non inverting amplifier should be 11, and it can be seen in the oscilloscope and simulation that the output waveform is 11 times amplified. Then as the name suggests, output will be non inverted as compared to input which means it will in phase with the input which is also evident in the graphs.

EXPERIMENT#3: Low Pass Filter

1 and 2 & 3

Lab 2 Experiment 3

$$A_V = \left\{ 1 + \frac{R_2}{R_1} \right\} V_{in}$$

$$C_1 = C_2 = C = 0.033 \mu F$$

$$F_H = 2 \text{ KHz}$$

$$F_H = \frac{1}{2\pi \sqrt{R_3 \times R_4 \times C_1 \times C_2}} \quad \text{given} = 2000 \times 10^3$$

$$R_1 = R_2 = R_3 = R_4 = R$$

$$R = \frac{1}{2\pi \times 2000 \times 2.7 \times 10^{-12}}$$

$$R = \frac{1}{2\pi \times 2000 \times 0.033 \times 10^{-6}} = 2.4 \text{ K}$$

$$R_3 = R_4$$

$$R_F = 0.586 \times R_{in}$$

$$A_V = A_F = 1 + \frac{R_F}{R_{in}} = 1 + \frac{R_2}{R_1}$$

$$C_1 = C_2 = 0.033 \mu F$$


$$R_3 = R_4 = 2.4 \text{ K}\Omega$$


$$R_F = R_2 = 5.86 \text{ K}\Omega \approx 5.6 \text{ K}\Omega$$



$$R_{in} = R_1 = 10 \text{ K}\Omega$$

output = $2 R_3$

input = R_1

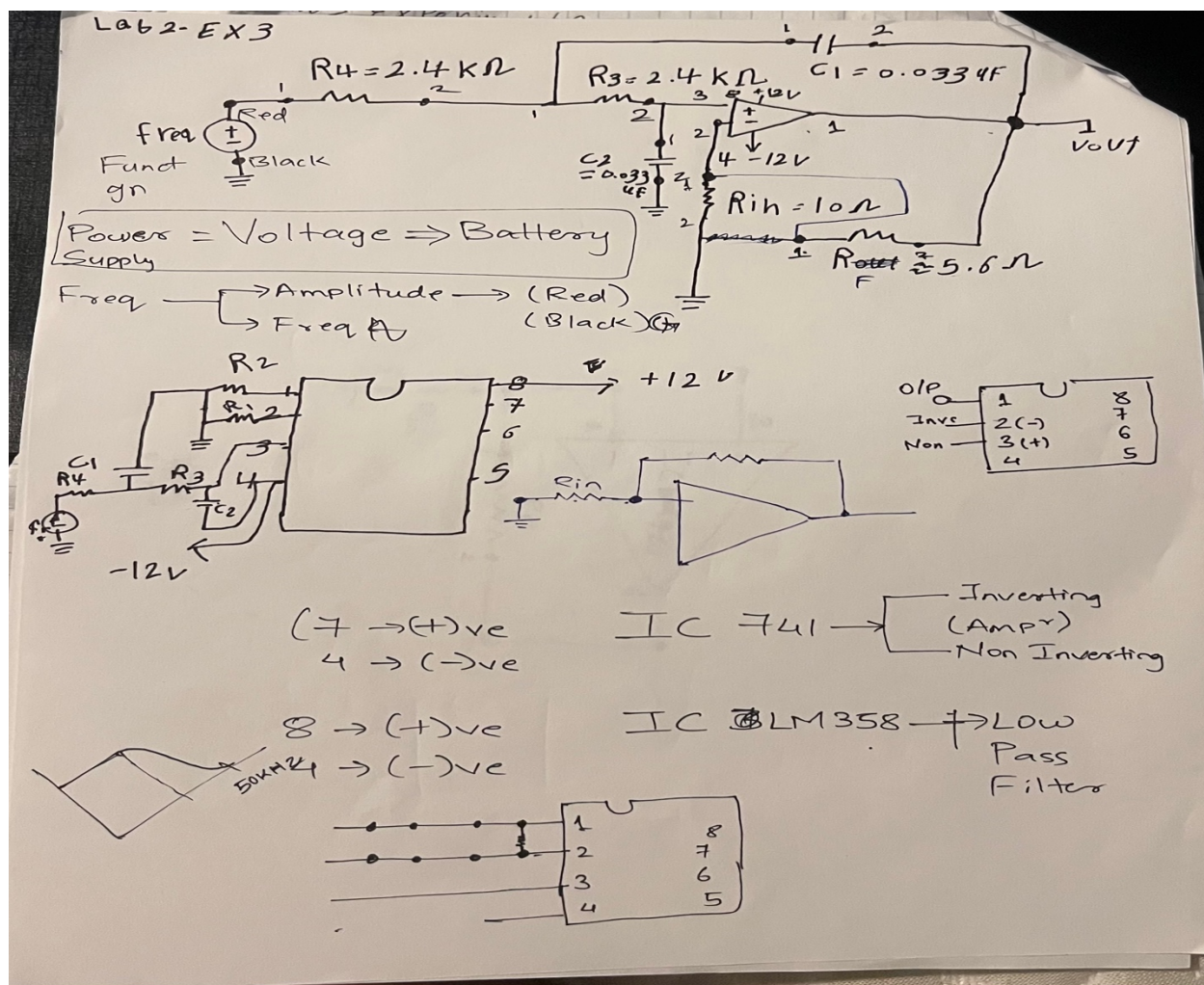

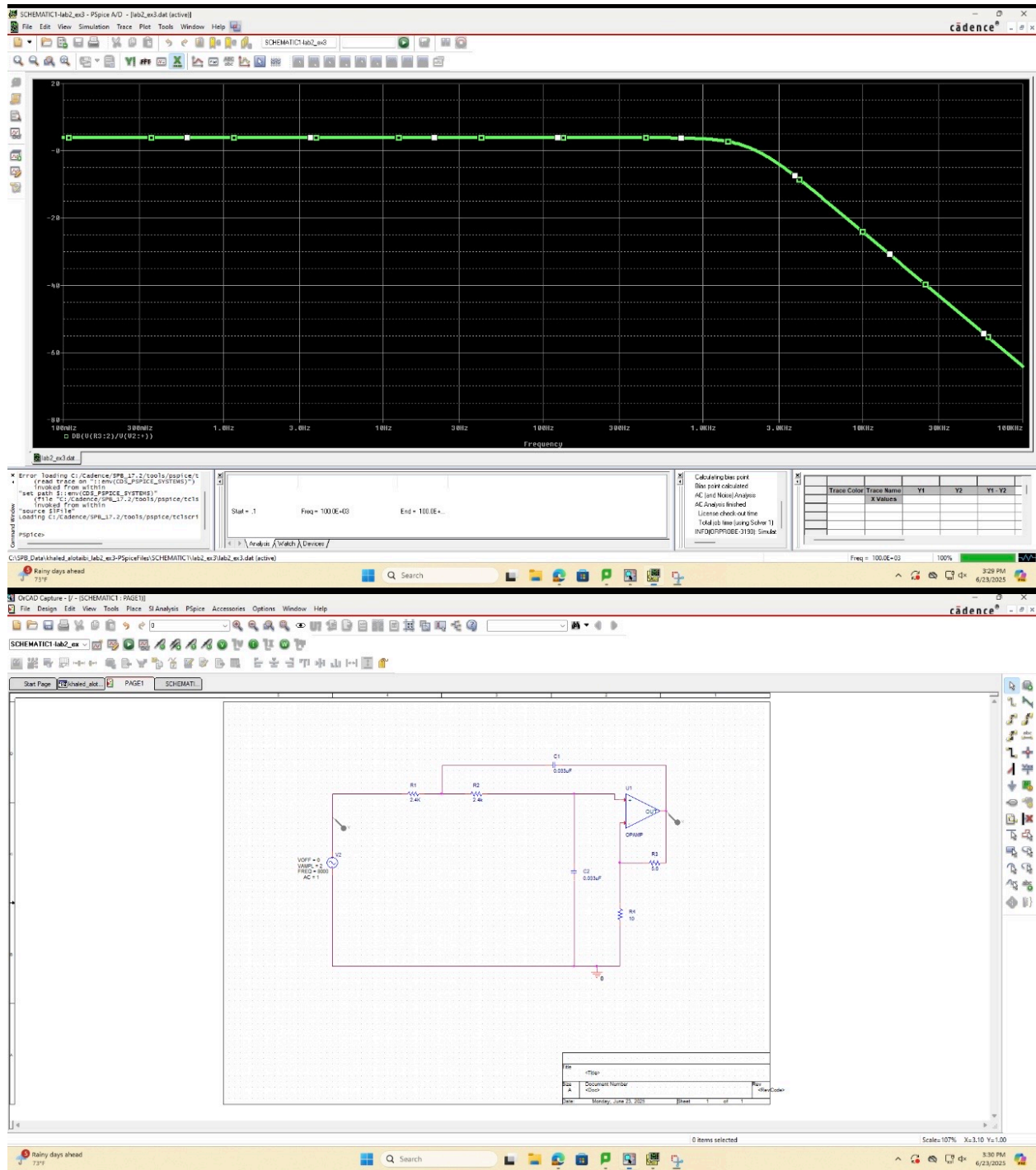

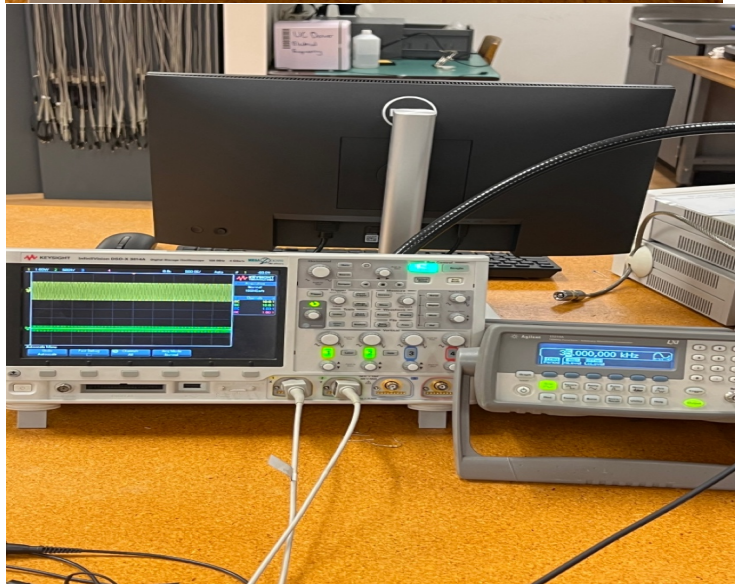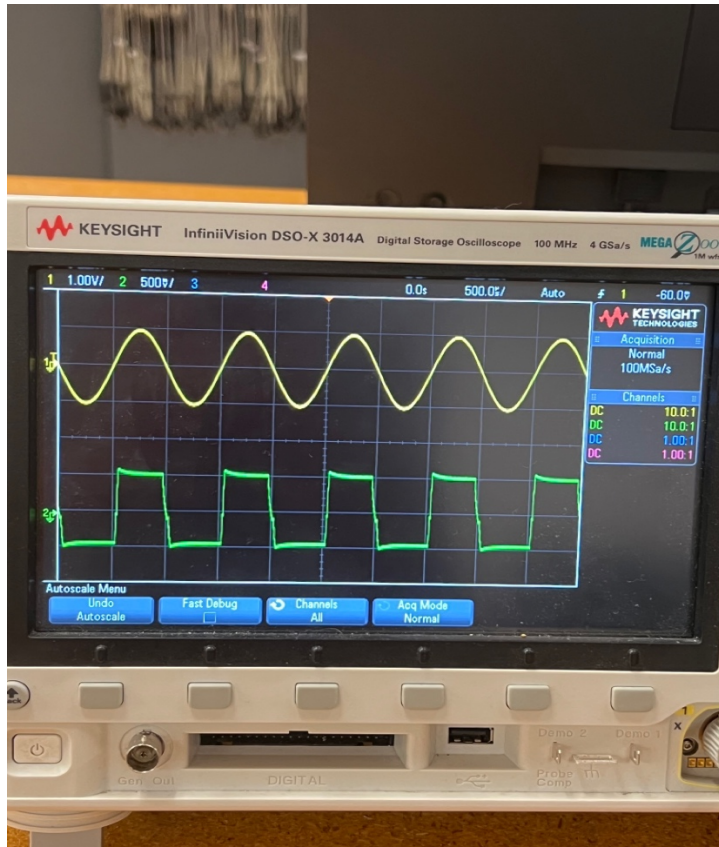

We calculated the values of resistors and capacitors based on the cutoff frequency of 2khz. For a low pass filter, whenever the signal of less than 2khz is passed, it will allow it. But when signal is out of the band, it will attenuate it.

EXPERIMENT#4: High Pass Filter

1-

Lab ²/₄ Experiment 4

$$A = \frac{1}{2\pi f_c} = \frac{1}{2\pi}$$

$$f_H = 5000 \text{ Hz}$$

$$R = \frac{1}{2\pi \times 5000 \text{ C}} = \frac{1}{2\pi \times 5000 \times 0.033 \times 10^{-6}}$$


$$= 964.5 = 1\text{K}$$

$$R_3 = 1\text{K} \quad R_4 = 1\text{K}$$

$$R_1 = 10$$

$$A_2 = 5.86 \approx 5.6$$

2&3-

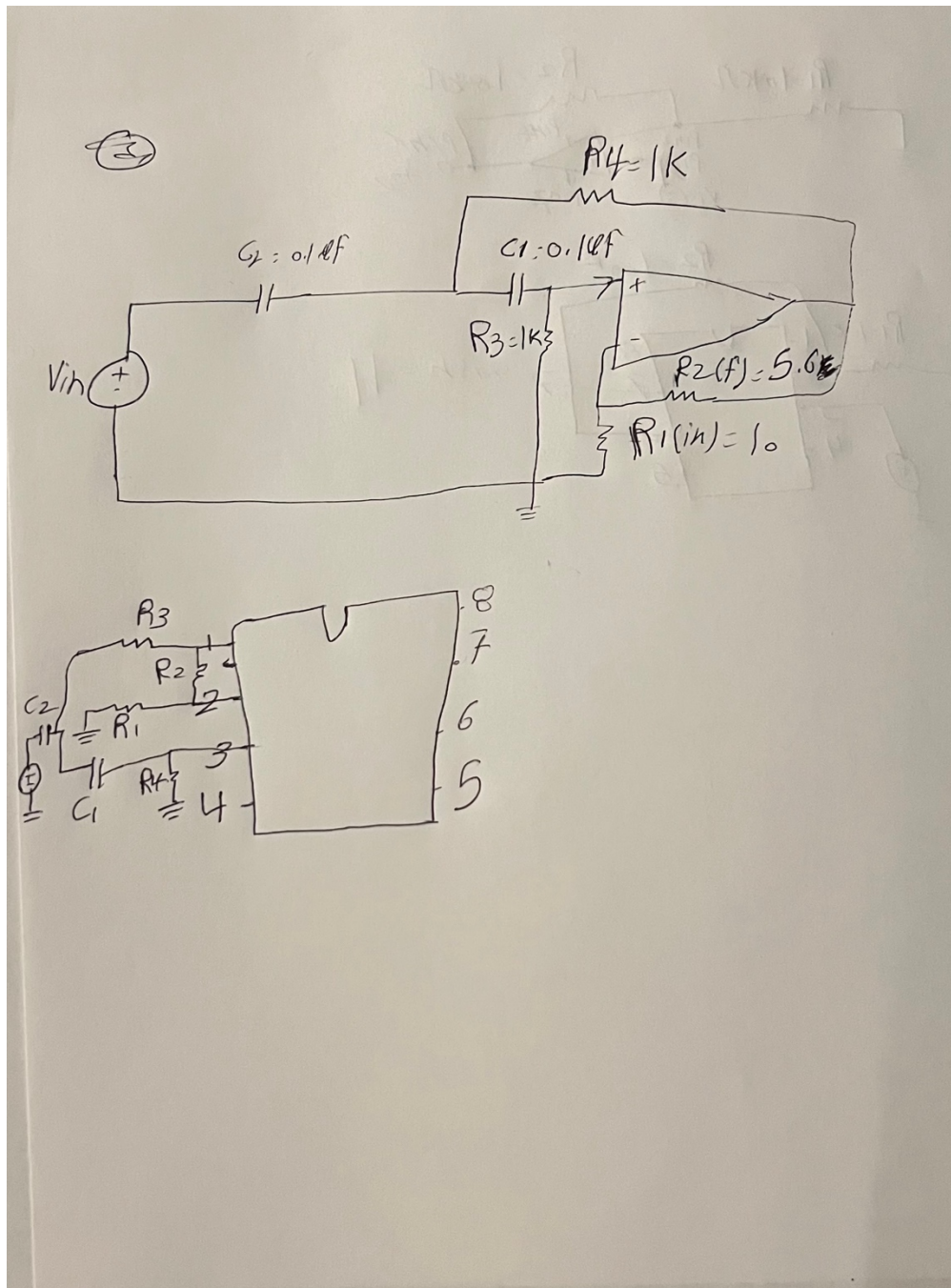

4-

